

1. <General Concept> (18%)

A. Briefly explain the following terms using a few sentences.


(a) (3pts) What is Combinational Loop?(b) (3pts) What is Boundary Optimization?(c) (3pts) What is Fault Coverage?

(d) (3pts) Explain how to reduce timing on critical path by pipelining technique?

(a) (20131009_CVSD_L6_Synthesizable_Coding.pdf 第 37 頁)

A combinational loop is a feedback loop without being synchronized by a register.


Fig: Combinational processes are looped

 

(b) (20131009_CVSD_L6_Synthesizable_Coding.pdf 第 9 頁)

Optimize **across** boundaries

 
1. Remove logic driving unconnected outputs
2. Remove redundant inverters
3. Propagate constants to reduce logic



(c) (20131030_CVSD_LA_Testing.pdf 第 28 頁)


$$\text{Fault coverage} = \frac{\text{number of detectable faults}}{\text{total number of possible faults}}$$

 (d) (20131009_CVSD_L5_Design_Guideline.pdf 第 15 頁)




 B. Setup time and hold time:

Assume that the timing characteristics of the two flip-flops in the circuit are the same. Their timing diagrams can be described as follows:



 If the circuit in the below operates at the clock frequency of **125MHz** without any timing violation:



(a) (3pts) Write the timing inequality for setup time.

(b) (3pts) Write the timing inequality for hold time.

$$(a) T_{\text{setup}} < T_{\text{clock}} - T_{\text{cq}} - T_{\text{logic}}$$

$$T_{\text{clock}} = 1000/125 = 8.0\text{ns} \quad T_{\text{logic}} = 4.0\text{ns} + 2.0\text{ns} = 6.0\text{ns} \quad T_{\text{cq}} = T_1 + T_2 = 1.0\text{ns}$$

$$\rightarrow T_{\text{setup}} < 8.0\text{ns} - 1.0\text{ns} - 6.0\text{ns} = 1.0\text{ns}$$

$$(b) T_{\text{cq,cd}} + T_{\text{logic,cd}} > T_{\text{hold}}$$

$$T_{\text{logic,cd}} = 3.0\text{ns} + 2.0\text{ns} = 5.0\text{ns} \quad T_{\text{cq,cd}} = T_1 = 0.5\text{ns}$$

$$\rightarrow 0.5\text{ns} + 5.0\text{ns} = 5.5\text{ns} > T_{\text{hold}}$$

2. <Verilog HDL -Code Debugging> (15%)

- A. (10pts) Identify syntax errors, correct them and explain: 1pt for each. Identify inappropriate code (or semantics errors), correct them and explain: 1pt for each.

```

module 2%shifter (out,clk, rst, in1, in2); (1.0pts) 分號結尾
    (1.0pts) 命名開頭必須為大小寫字母或底線(_)
    input clk, rst;
    input [15:0] in1;
    input [2:0] in2;


    output [15:0] out; reg [15:0] out; (1.0pts) Register Output

    reg[15:0] shift; wire [15:0] shift; (1.0pts) Continuous Assignment 的對象必須為 Wire
    assign shift = in1 >> in2;
    /* variable shifter*/ (1.0pts) 少一個星號必須補上

    always @(posedge clk or posedge rst) begin (1.0pts) 少一個 begin
    if(!rst) out = 16'd0; if(rst) out <= 16'd0; (2.0pts) (1) High Level 重置 (2) Non-blocking
    else out = shift; else out <= shift; (1.0pts) (1) Non-blocking
    end

    endmodule (1.0pts) (1) endmodule 沒有 s
  
```

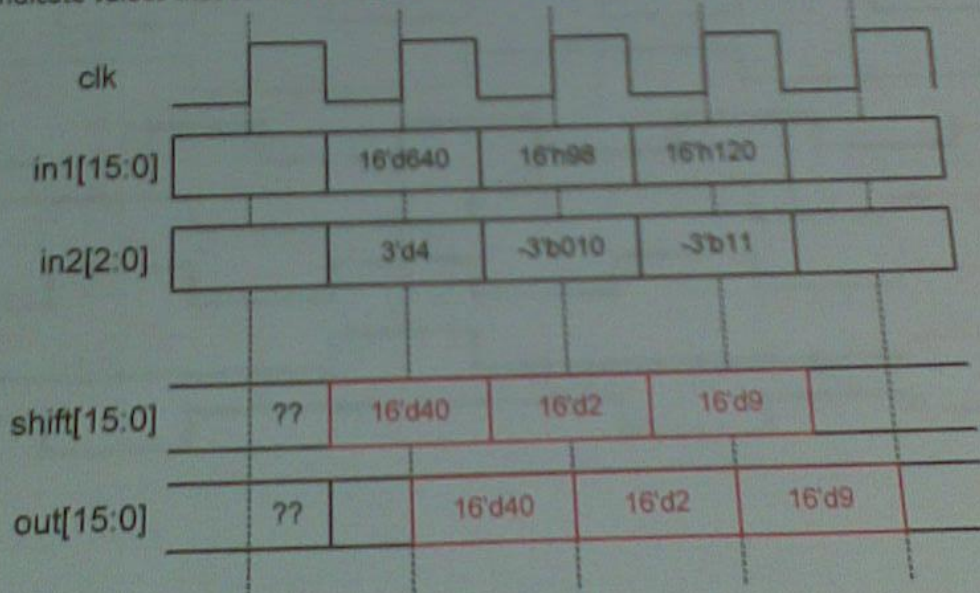- B. (5pts) Finish the waveform below based on the circuit in part A. Note that you should use the decimal number representation to answer (such as 16'd0). Use "xx" to indicate values that cannot be determined from the information given.




3. <Verilog HDL-Simulation> (10%)

The bellow is the behavior code from a testbench. Draw the waveform before 80ns.


```
always@(posedge clk) begin
    c <= a;
    d <= #5 a^b;
    #5 e <= c;
    f <= @(negedge clk) a & d;
    @(negedge clk) g <= a | d;
end
```

Red Line: Unknown

 

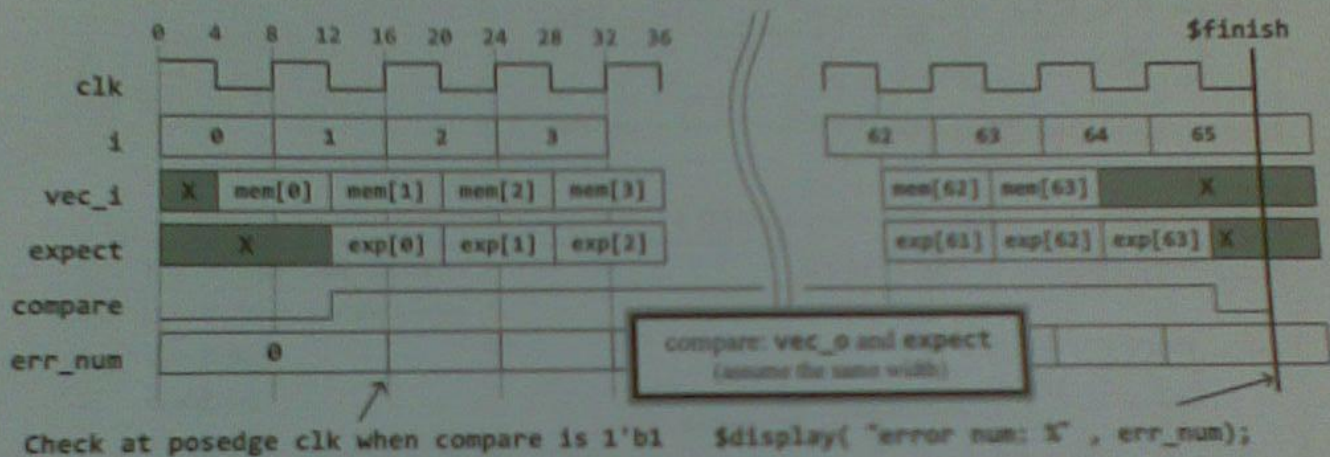4. <Verilog HDL –Testbench Writing> (15%)

Complete the key initial/always blocks testbench to generate the following waveform and control the progress of simulation. Assume every necessary identifier has been declared, and the array of `mem` and `exp` is pre-loaded in another initial block at zero time. (Hint: Generate `clk` and `i` independently. Use different initial/always constructs for each of the rest signals: `vec_i`, `expect`, `compare`, and `err_num`. Remember to call system tasks at final).



```
`define Cycle = 8;
```

```
`define HCycle = 4;
```

```
initial begin
```

```
    clk = 1;
```

```
    i = 0;
```

```
    err_num = 0;
```

```
end
```

```
always begin
```

```
    #(`HCycle) clk = ~clk;
```

```
    #(`Cycle) i = i+1;
```

```
end
```



```
always@(negedge clk) begin
```

```
    vec_i = mem[i];
```

```
    if(i != 0)
```

```
        expect <= exp[i-1];
```

```
    if(i == 0 || i == 65)
```

```
        compare <= 0;
```

```
    else
```

```
        compare <= 1;
```

```
end
```

```
always@(posedge clk) begin
```

```
    if( (compare == 1) && (vec_0 == expect) )
```

```
        error_num <= error_num + 1;
```

```
end
```

```
always@(posedge clk) begin
```

```
    if(i == 65) begin
```

```
        $display("error num: %", err_num);
```

```
        $finish;
```

```
    end
```

```
end
```


5. <Logic Synthesis + Blocking & Non-Blocking> (10%)

In the following table, the left column show some pieces of Verilog RTL code. Please draw the corresponding circuits in the right column. You can use AND, OR, NAND, NOR, XOR, XNOR, NOT, MUX in the circuit diagram.

(a) Verilog Code (2pts)	Circuit Diagram
<pre> always @(posedge clk) begin A <= INPUT; B <= A ^ D; C <= B; D <= C ^ D; end </pre>	
(b) Verilog Code (2pts)	Circuit Diagram
<pre> always @(posedge clk) begin A = INPUT; B = A ^ D; C = B; D = C ^ D; end </pre>	
(c) Verilog Code (3pts)	Circuit Diagram
<pre> always@(A or B or C) begin if (C) D = A & B; end </pre>	
(d) Verilog Code (3pts)	Circuit Diagram
<pre> always@(posedge clk) begin if (C) D <= A & B; end </pre>	

6. <Synthesis Issues> (10%)


- (a) (6pts) The "multiple design instance" warning message results from using the same HDL description to represent more than one design instance. How would you handle it? Explain the property of each method. (Hint: There are three methods)

Don't touch
Ungroup
Uniquify

- (b) (2pts) If we specify the clock to be 5.0ns during synthesis, the timing that the constraints has been met. However, the gate-level simulation 4.0ns with one set of test data. Is this possible? Why or why not?

有可能。因為合成時所關心的是電路中的 Critical Path，當電路合成 Constrains，所代表的是 Critical Path Delay 可以落在 5.0ns，其餘 Path 會在 5.0ns 以內。所以當我們使用的 Test Data 有某一組走的不是 Critical Path 在 4.0ns 的 Timing 之下仍有可能 Pass。

 - (c) (2pts) Use a simple example to explain how retiming improves the performance of a sequential circuit.



Computer-Aided VLSI System Design Graduate Institute of Electronics Engineering, NTU

Uniquify Method

- Create a unique design for each instance, even if it is resolved from identical reference. 即使是相同的 reference，也要用不同的 name 命名。
- Hierarchy of design is preserved. design 的層次關係保持不變。
- Hierarchy/Uniquify/Hierarchy

Pros and cons:

- More memory
- Longer compile time
- Better performance

Code: `do_shell uniquify` 建議不用的指令

Computer-Aided VLSI System Design Graduate Institute of Electronics Engineering, NTU

Compile-once-don't-touch method

- Two steps: 先合 C.O. → 合 B.T. 時，對 C.O. → don't-touch
- Pre-compile the sub-blocks 各自先合成，已經固定，傳資料給主塊。
- Set these sub-blocks as don't_touch for compiling entire design
- Attributes/Optimization Directives/Design & set the Don't Touch

Pros and cons:

- Less memory
- Shorter compile time

Code: `do_shell set_dont_touch [cell_list]`

Computer-Aided VLSI System Design Graduate Institute of Electronics Engineering, NTU

Ungroup Method 整個打散 (letting)

- The same effect as uniquify method but it removes hierarchical levels
- Hierarchy of design is broken.
- Attributes/Optimization Directives/Design & set the Ungroup


Pros and cons:

- More memory requirement than Compile-once-don't-touch
- Longer compile time than Compile-once-don't-touch method
- Better performance to optimize boundary logic
- Removing user-defined design hierarchy

Code: `do_shell ungroup [cell_list]` 原本的 hierarchy 消失

 7. <Timing Analysis> (15%)


Calculate the arrival time, required time, and slack at each gate output. Assume the delays of NAND gates and NOR gates are 4ns and 3ns, respectively. The arrival time at primary inputs is 0ns, and the required time at primary outputs is 12ns.




X1:	Arrival	<u>0ns</u>	; Required	<u>-2ns</u>	; Slack	<u>-2ns</u>
X2:	Arrival	<u>0ns</u>	; Required	<u>-2ns</u>	; Slack	<u>-2ns</u>
X3:	Arrival	<u>0ns</u>	; Required	<u>-3ns</u>	; Slack	<u>-3ns</u>
X4:	Arrival	<u>0ns</u>	; Required	<u>-3ns</u>	; Slack	<u>-3ns</u>
Y1:	Arrival	<u>3ns</u>	; Required	<u>1ns</u>	; Slack	<u>-2ns</u>
Y2:	Arrival	<u>4ns</u>	; Required	<u>1ns</u>	; Slack	<u>-3ns</u>
			Or Required	<u>5ns</u>	; Slack	<u>1ns</u>
Y3:	Arrival	<u>8ns</u>	; Required	<u>5ns</u>	; Slack	<u>-3ns</u>
Y4:	Arrival	<u>11ns</u>	; Required	<u>8ns</u>	; Slack	<u>-3ns</u>
Z1:	Arrival	<u>15ns</u>	; Required	<u>12ns</u>	; Slack	<u>-3ns</u>
Z2:	Arrival	<u>15ns</u>	; Required	<u>12ns</u>	; Slack	<u>-3ns</u>

8. <Design for Testability> (12%)

 A. Given the circuit below, please answer the following questions.



- (a) (2pts) How many stuck-at faults (SAF) are in the circuit?
 (b) (4pts) Generate all possible test patterns for fault $n_1/0$.
 (c) (4pts) Generate all possible test patterns for fault $n_2/0$.
 (d) (2pts) What is the fault coverage for patterns generated for fault $n_2/1$?

 (a) $8 \times 2 = 16$ (b) Activation: $n_1 = 1 \rightarrow A_3 = 0 \& A_2 = 0$ Propagation: $n_1 = 1 \rightarrow (n_2, A_2) = (1,0) (0,1) (0,0) \rightarrow (A_1, A_0) = (0,0) \text{ or } (1,1) (1,0)$ Patterns $(A_0, A_1, A_2, A_3) : (0,0,0,0) (1,1,0,0) (1,0,0,0)$ (c) Activation: $n_2 = 1 \rightarrow A_1 = 0 \& A_0 = 1$ Propagation: $n_2 = 1 \rightarrow A_3 = 0 \& A_2 = 0$ Patterns $(A_0, A_1, A_2, A_3) : (1,0,0,0)$ (d) Activation: $n_3 = 0 \rightarrow n_2 = 1 \& A_0 = 1 \rightarrow A_1 = 0 \& A_0 = 1$ Propagation: $n_3 = 1 \rightarrow A_3 = 0 \& A_2 = 0$ Patterns $(A_0, A_1, A_2, A_3) : (1,0,0,0)$  $n_3 = 0 \rightarrow$ faults cannot propagate through n_1 , remove $\{n_1/0, A_2/1, A_3/1\}$ FC = 5/16 (detect 5 faults: $\{A_0/0, A_1/1, n_2/0, n_3/1, Y/0\}$ out of 16 faults)